

AUDIO AMPLIFIER

CMONO


-ee23btech11042


Aim : To design and implement a simple audio amplifier circuit capable of amplifying audio signals.

equipment used :

- LM 386 IC
- Bread board
- 10MF capacitor (x 3)
- 220MF, 4.7nF, 100MF, 104pF
- 10- Ω resistor
- B-10K potentiometer
- Audio jack
- ROHS 8- Ω speaker

Circuit diagram :

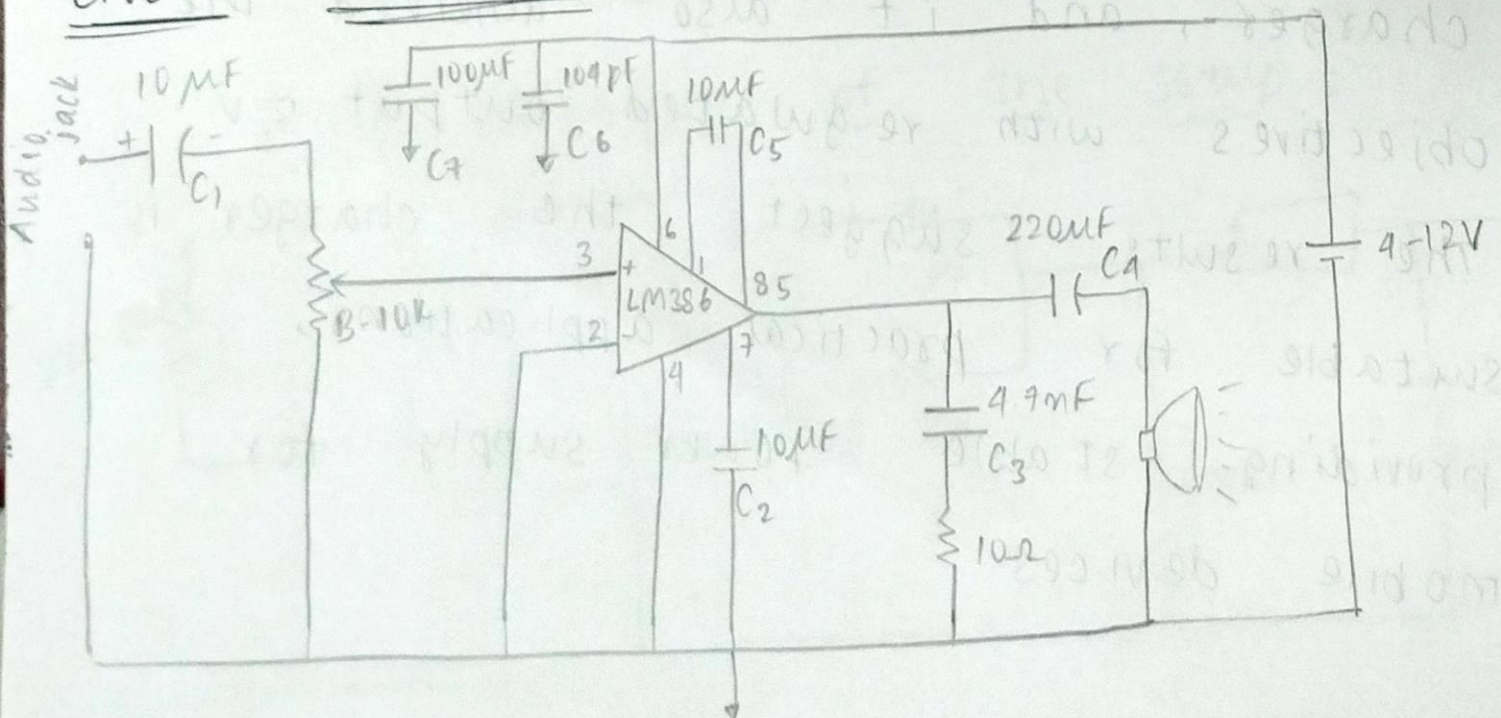

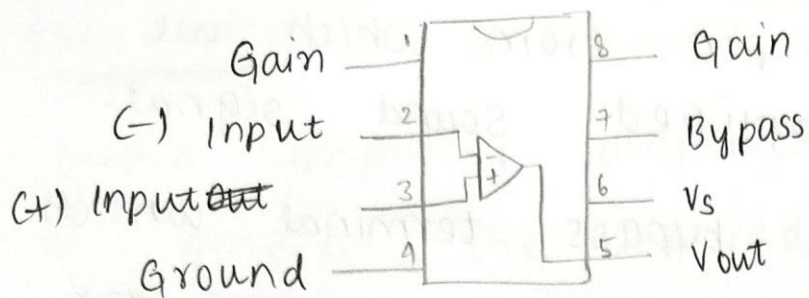

Functions of various components:

i) LM 386 : It is a low voltage audio amplifier used in music devices like radio, guitar... etc.

→ It's gain is 20-200.

→ It has a wide range of supply voltage range 4-12V.

→ Pin 1, 8 : Gain control pins. The default gain 20 can be increased to 200 by using appropriate capacitors. We used 10 μ f to get the highest gain [200].

→ Pin 2, 3 : Input pins for sound signals. Negative input terminal is connected to ground. Sound signal is fed to positive input terminal by a potentiometer which acts as volume control knob.

→ Pin 4, 6 : power supply pins. pin 6 is connected to V_{cc} and pin 4 to ground.

- pin 5: output pin from which we get the amplified sound signal
- pin 7: It is a bypass terminal which is grounded using a capacitor for stability.
- C₁: It is used to remove DC component of input signal allowing only AC component ~~to~~ to be fed further.
- C₂: connected to Bypass terminal of IC for stability of the circuit.
- C₃, 10-2: It is a filter called 'Zobel Network' used to remove sudden high frequency oscillations / noise.
- C₄: removes DC component of output signal allowing only AC component to be fed to the speaker.
- C₅: used to adjust gain
- C₆, C₇: used to reduce the noise of the ~~output sound~~ ^{input DC voltage}.
- potentiometer: acts as a volume control knob by adjusting the resistance.

Conclusion : In conclusion, the designed audio amplifier amplifies effectively. It achieves the desired amplification with adjustable volume control. This project demonstrates a basic yet effective approach of audio amplification suitable for various music devices

x